

Practical VHDL Samples 2

The following is a list of files used as examples in the ESD3 lectures.

The files are included overleaf with simulations and post-synthesis schematics where applicable.

Source Name	Entity Name	Description	Synthesisable?	Comments
ssmach.vhd	ssmach	Simple State Machine		Implements a basic state machine with no outputs. Illustrates the basic structure of a state machine in VHDL.
ssmach2.vhd	ssmach2	State Machine With Outputs	✓	Implements a simple state machine with outputs. Illustrates outputs being a function of present state etc.
upcount.vhd	upcounter	Simple counter.	✓	Demonstrates the use of the numeric_std package for arithmetic. Also demonstrates the use of conversion routines present in numeric_std for conversion to std_logic.
rom.vhd	rom	ROM	✓	Implements a basic 16 address by 5 bit ROM. Illustrates the creation of memory structures and also arrays in VHDL.
testalu.vhd	testbench_alu	Structural schematic.		Illustrates the use of structural VHDL for schematic designs.

```
-- Title      : Simple State Machine Implementation in VHDL
-- Project    : Digital Design IV
-- File       : ssmach.vhd
-- Author     : <Craig Slorach@HANDEL>
-- Created    : 1999/02/17
-- Last modified : 1999/02/17
-- Description :
-- Implements a simple state machine with no outputs in VHDL
-- Modification history :
-- 1999/02/17 : created

-- NOTE THIS DESIGN IS FOR DEMONSTRATION/ SIMULATION PURPOSES ONLY- IT CANNOT
-- BE SYNTHESISED SINCE THERE ARE NO SYSTEM OUTPUTS AND AS SUCH THE
-- OPTIMISATION STEP IN SYNTHESIS WILL YIELD NO CIRCUIT !

library ieee;
use ieee.std_logic_1164.all;

entity SSMACH is
    port (input : in std_logic;      -- system input to start the system
          clk,reset : in std_logic);  -- clock and reset inputs
end SSMACH;

-- purpose: Implement main architecture for SSMACH
architecture BEHAVIOR of SSMACH is
    type STATES is (START, OPENED, CLOSED); -- possible states
    signal PRESENT_STATE : STATES;          -- present state

begin -- BEHAVIOR

    -- purpose: Main process
    process (clk, reset)

        begin -- process

            -- activities triggered by asynchronous reset (active high)
            if reset = '1' then

                PRESENT_STATE <= START;      -- default state

            -- activities triggered by rising edge of clock
            elsif clk'event and clk = '1' then

                case PRESENT_STATE is


                    when START =>
                        if INPUT='1' then
                            PRESENT_STATE <= OPENED;
                        else
                            PRESENT_STATE <= START;
                        end if;

                    when OPENED =>
                        PRESENT_STATE <= CLOSED;

                    when CLOSED =>
                        PRESENT_STATE <= START;

                    when others =>
                        PRESENT_STATE <= START;

                 end case;
            end if;
        end process;
    end BEHAVIOR;
```



```

-----
-- Title       : Simple State Machine Implementation (with outputs) in VHDL
-- Project      : Digital Design IV
-----
-- File        : ssmach2.vhd
-- Author       : <Craig Slorach@HANDEL>
-- Created      : 1999/02/17
-- Last modified : 1999/02/17
-----

```

```

-- Description :
-- Implements a simple state machine with outputs in VHDL
-----
-- Modification history :
-- 1999/02/17 : created
-- 2000/01/13 : Updated for default output behaviour
-----

```

```

library ieee;
use ieee.std_logic_1164.all;

```

```

entity SSMACH2 is

```

```

    port (input      : in  std_logic;    -- system input to start the system
          output      : out std_logic;    -- system output
          clk, reset  : in  std_logic);   -- clock and reset inputs

```

```

end SSMACH2;

```

```

-- purpose: Implement main architecture for SSMACH2
architecture BEHAVIOR of SSMACH2 is

```

```

    type STATES is (START, OPENED, CLOSED); -- possible states
    signal PRESENT_STATE : STATES;           -- present state

```

```

begin -- BEHAVIOR

```

```

    -- purpose: Main process
    process (clk, reset)
    begin -- process

```

```

        -- activities triggered by asynchronous reset (active high)
        if reset = '1' then
            PRESENT_STATE <= START;           -- default state
            OUTPUT        <= '0';

```

```

        -- activities triggered by rising edge of clock
        elsif clk'event and clk = '1' then

```

```

            OUTPUT        <= '0';           -- default output
            PRESENT_STATE <= OPENED;        -- default state

```

```

            case PRESENT_STATE is

```

```

                when START =>
                    if INPUT = '1' then
                        PRESENT_STATE <= OPENED;
                        OUTPUT        <= '1';
                    else
                        PRESENT_STATE <= START;
                        OUTPUT        <= '0';
                    end if;

```

```

                when OPENED =>
                    PRESENT_STATE <= CLOSED;
                    OUTPUT        <= '0';

```

```

                when CLOSED =>
                    PRESENT_STATE <= START;
                    OUTPUT        <= '0';

```

```


                when others =>
                    PRESENT_STATE <= START;
                    OUTPUT        <= '0';


```

```

            end case;
        end if;
    end process;
end BEHAVIOR;

```

 


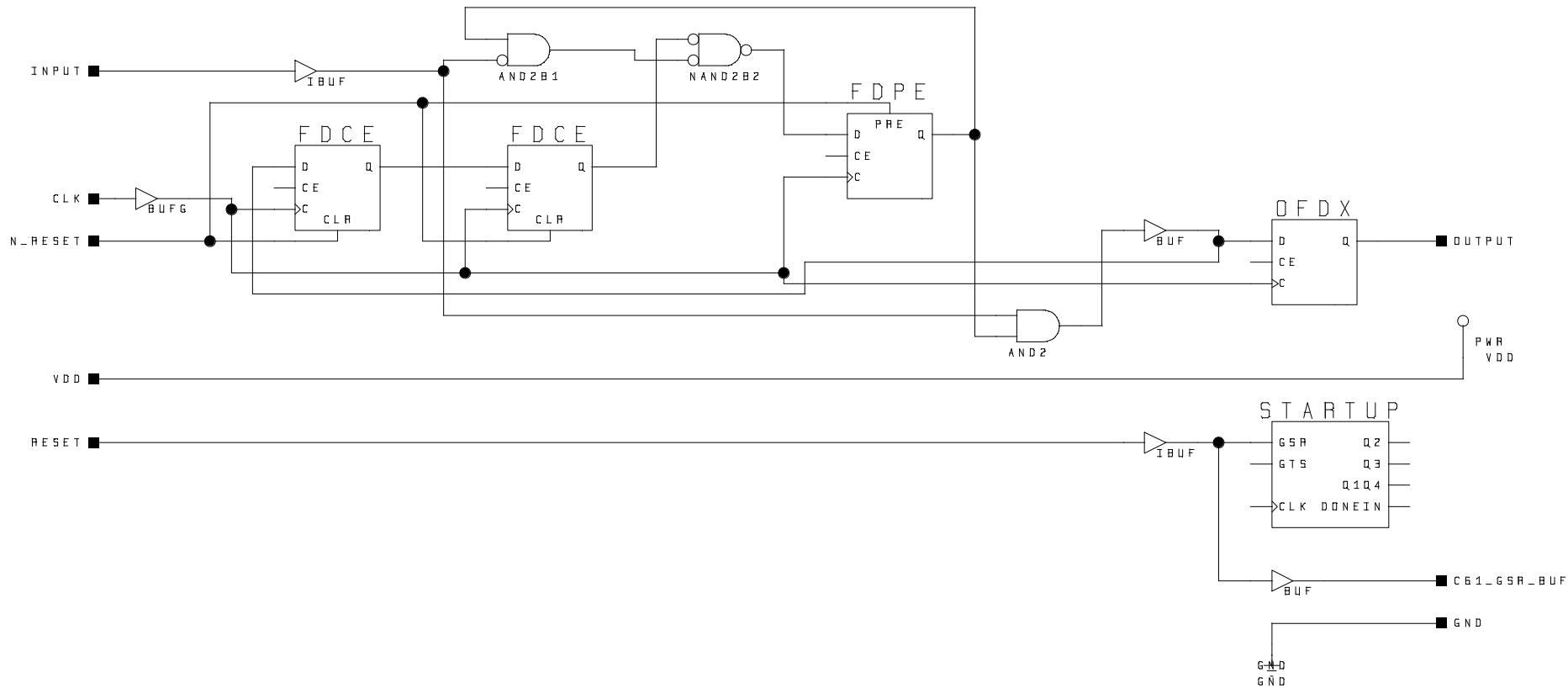

```
-- Title      : Simple counter in VHDL
-- Project    : Digital Design IV
--
-- File       : upcounter.vhd
-- Author      : <Craig Slorach@HANDEL>
-- Company    :
-- Last update: 2000/01/13
-- Platform   :
--
-- Description: Implements a simple counter in VHDL which counts up only
--              when an input 'inc' = '1'
--
-- Revisions  :
-- Date       Version  Author  Description
-- 2000/01/13  1.0      Craig Slorach  Created
--
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity UPCOUNTER is
    port (
        inc      : in  std_logic;           -- increment input
        count    : out std_logic_vector (3 downto 0); -- output
        clk, reset : in  std_logic);        -- clock and reset
end UPCOUNTER;

architecture BEHAVIOR of UPCOUNTER is
    signal internal_count : unsigned (3 downto 0); -- internal counter
begin -- BEHAVIOR
    -- purpose: Main process
    -- type    : sequential
    -- inputs  : clk, reset, inc
    -- outputs : internal_count
    process (clk, reset)
    begin -- process
        if reset = '1' then -- asynchronous reset (active high)
            internal_count <= "0000";
        elsif clk'event and clk = '1' then -- rising clock edge
            if inc = '1' then
                if internal_count = "0100" then
                    internal_count <= "0000"; -- reset back
                else
                    internal_count <= internal_count + 1; -- increment
                end if;
            else
                null;
            end if;
        end if;
        -- drive the counter output with the internal value
        count <= std_logic_vector(internal_count);
    end process;
end BEHAVIOR;
```

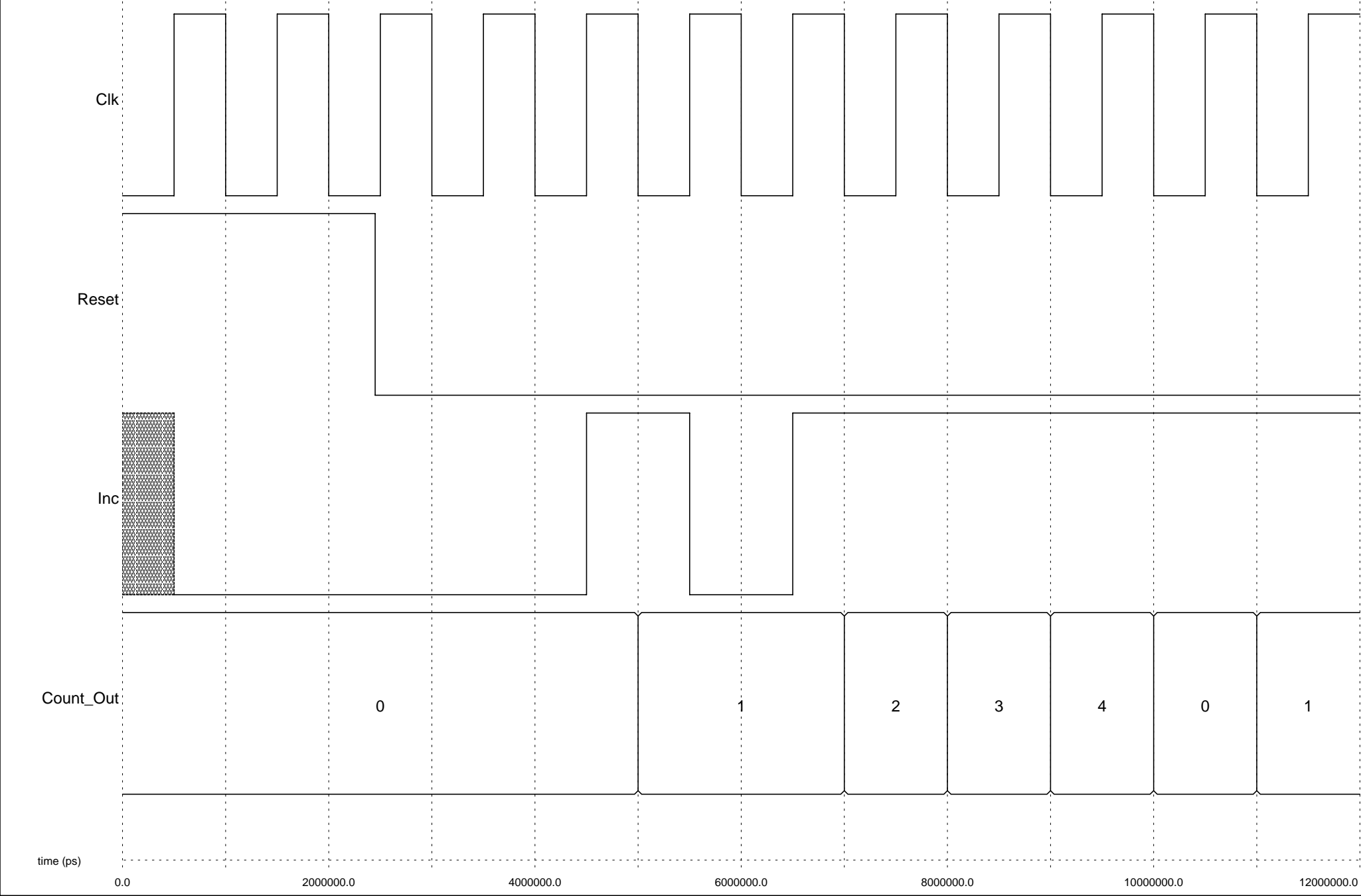


```
-- Title      : ROM Implementation in VHDL
-- Project    : Digital Design IV
--
-- File       : rom.vhd
-- Author     : <Craig Slorach@HANDEL>
-- Company    :
-- Last update: 2000/01/13
-- Platform   :
--
-- Description: Implements a 16 x 5 ROM in VHDL with a combinational logic
--              approach.
--
-- Revisions  :
-- Date       Version  Author  Description
-- 2000/01/13  1.0     Craig Slorach  Created
--
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity ROM is
    port (
        ADDR : in  std_logic_vector (3 downto 0);  -- address input
        DOUT : out std_logic_vector (4 downto 0));  -- data output
end ROM;

architecture BEHAVIOR of ROM is

    type ROMTABLE is array (0 to 15) of std_logic_vector (4 downto 0);
    -- internal table

    constant romdata : romtable := (

        "10101",          -- data for address 0
        "11111",          -- data for address 1
        "10101",
        "11110",
        "10110",
        "10101",
        "11010",
        "10010",
        "10110",
        "11101",
        "10110",
        "10111",
        "00110",
        "11101",
        "10010",
        "10110"          -- data for address 15
    );

begin  -- BEHAVIOR

    -- purpose: Main process
    -- type   : combinational
    -- inputs : ADDR
    -- outputs: DOUT
    process (ADDR)
    begin  -- process

        DOUT <= romdata(to_integer(unsigned(ADDR)));

    end process;
end BEHAVIOR;
```

```
--Netlist:
--Library=dd49900lab1,Cell=testbench_alu,View=schematic
--Time:Thu Dec 9 11:39:48 1999
--By:craigs

LIBRARY ieee;
USE ieee.std_logic_1164.all;
ARCHITECTURE schematic OF testbench_alu IS
    COMPONENT alu
        PORT(
            carryout : OUT std_logic;
            result : OUT std_logic_vector(3 DOWNTO 0);
            a : IN std_logic_vector(3 DOWNTO 0);
            b : IN std_logic_vector(3 DOWNTO 0);
            clk : IN std_logic;
            inst : IN std_logic_vector(1 DOWNTO 0);
            rst_n : IN std_logic
        );
    END COMPONENT;

    COMPONENT stim_alu
        PORT(
            stim_a : OUT std_logic_vector(3 DOWNTO 0);
            stim_b : OUT std_logic_vector(3 DOWNTO 0);
            stim_clock : OUT std_logic;
            stim_inst : OUT std_logic_vector(1 DOWNTO 0);
            stim_reset : OUT std_logic
        );
    END COMPONENT;

    SIGNAL reset : std_logic;
    SIGNAL clock : std_logic;
    SIGNAL inst : std_logic_vector(1 DOWNTO 0);
    SIGNAL a : std_logic_vector(3 DOWNTO 0);
    SIGNAL b : std_logic_vector(3 DOWNTO 0);

    FOR ALL: alu USE ENTITY dd4lab1.alu(behavior);
    FOR ALL: stim_alu USE ENTITY dd4lab1.stim_alu(behavior);

BEGIN

    \I2\ : alu
        PORT MAP(
            carryout => alucarryout,
            result(3 DOWNTO 0) => aluout(3 DOWNTO 0),
            a(3 DOWNTO 0) => a(3 DOWNTO 0),
            b(3 DOWNTO 0) => b(3 DOWNTO 0),
            clk => clock,
            inst(1 DOWNTO 0) => inst(1 DOWNTO 0),
            rst_n => reset
        );

    \I1\ : stim_alu
        PORT MAP(
            stim_a(3 DOWNTO 0) => a(3 DOWNTO 0),
            stim_b(3 DOWNTO 0) => b(3 DOWNTO 0),
            stim_clock => clock,
            stim_inst(1 DOWNTO 0) => inst(1 DOWNTO 0),
            stim_reset => reset
        );

END schematic;
```